

L02 – Distribution Network Power Flow

Foundations Lecture Series

Course Instructor

Microgrid 3-phase Security AI Project

Foundations Lecture 2

Keywords: radial topology, R/X ratio, backward/forward sweep, LinDistFlow, voltage rise

Lecture roadmap


- 1 Why transmission and distribution need different treatments
- 2 Radial topology and the Backward/Forward Sweep (BFS) algorithm
- 3 Worked BFS example on a 4-bus feeder
- 4 LinDistFlow: when a linear voltage drop is enough
- 5 DER on distribution feeders: voltage rise and reverse flow
- 6 Microgrids and the bridge to L04 (unbalanced PF)

Prerequisite

L01 – you should be comfortable with Y_{bus} , Newton-Raphson, per-unit, and `pp.runpp`.


Two very different worlds

Transmission network

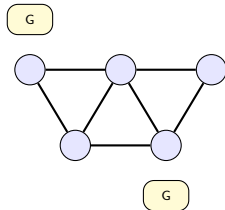

Meshed. Multiple generators. 110–765 kV.

Distribution feeder

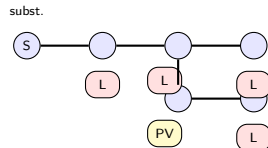

Radial. One source. 0.4–35 kV. Many small loads + DER.

Why we cannot just reuse L01 directly

The math from L01 still applies in principle, but every *practical* assumption (balanced phases, low R/X, mesh topology, stable convergence) is weaker or wrong on distribution feeders.

Side-by-side comparison

	Transmission	Distribution
Voltage level	110 kV – 765 kV	0.4 kV – 35 kV
Topology	Meshed (loops)	Radial (tree)
Line R/X ratio	0.1 – 0.3	1 – 3 (sometimes higher)
Loads	Aggregated, balanced	Many small, often single-phase
Generators	Large central, three-phase	PV / BESS / EV, often single-phase
Phase symmetry	Usually fine	Rarely true
Direction of flow	One direction historically	Bi-directional with DER
Typical solver	Newton-Raphson (NR)	BFS, BFSW, sometimes NR

Reading this table

Every row is a reason this lecture exists. We will see each effect concretely on a small example before the lecture ends.

The R/X problem – with numbers

For a single radial line carrying load $P + jQ$ to the next bus, the voltage drop is approximately

$$\Delta V = V_i - V_j \approx \frac{R P + X Q}{V} \quad (\text{small-angle, low-loss approximation})$$

Take a load of $P = 1.0$ pu, $Q = 0.3$ pu at $V \approx 1$ pu:

	R (pu)	X (pu)	ΔV (pu)
Transmission line	0.01	0.10	$0.01 + 0.03 = \mathbf{0.04}$
LV distribution feeder	0.10	0.05	$0.10 + 0.015 = \mathbf{0.115}$

The consequence

On the LV feeder ΔV is *three times larger and* dominated by the active-power term. The classical “ P moves θ , Q moves $|V|$ ” decoupling from textbook transmission analysis no longer holds.

Why this matters for solvers

Newton-Raphson assumes...

- Reasonable initial guess (flat start works)
- Well-conditioned Jacobian
- Modest voltage drops
- Mostly inductive lines (low R/X)

On long, heavily-loaded LV feeders, the Jacobian can become ill-conditioned and NR may not converge from a flat start.


Specialized distribution methods exploit...

- Radial topology (a tree, not a graph)
- Single path from each bus to the source
- Easy KCL summation along that path
- No need to factor a large Jacobian

The most common is BFS

Backward/Forward Sweep: walk the tree twice per iteration. Simple. Robust on long radial feeders.

What “radial” means

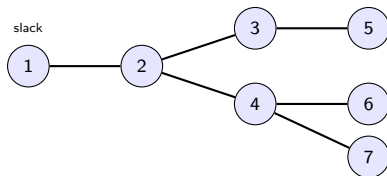


Properties of a radial network

- Exactly one path from any bus back to the slack
- No loops
- Each non-slack bus has exactly one “parent”
- Looks like a tree rooted at the substation

Why this is exploitable

- Currents downstream of bus k all flow through one branch
- KCL at each bus is a simple sum
- KVL along each branch is one equation
- No matrix inversion needed

Backward/Forward Sweep: the intuition

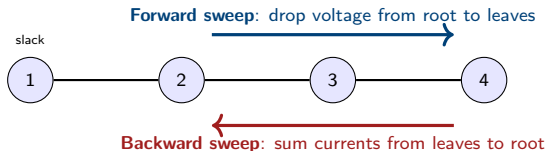

Two-line summary

Backward: given a voltage estimate, compute the load current at each bus and *sum* currents flowing toward the substation.

Forward: given the branch currents, walk from the slack outward and *subtract* the voltage drop on each branch.

Repeat backward + forward until the voltage estimate stops changing.

BFS algorithm in pseudocode

Inputs: radial topology, line impedances z_{ij} , complex loads S_i , slack voltage V_1 .

Initialize: $V_i \leftarrow V_1$ for all i (flat start).

```
while not converged:
    # ---- Backward sweep ----
    # Walk from leaves to root, in reverse topological order
    for bus i in reverse_order:
        I_load_i = conj(S_i / V_i)
        I_branch[parent(i) -> i] = I_load_i + sum(I_branch[i -> child])

    # ---- Forward sweep ----
    # Walk from root outward, in topological order
    for bus j in forward_order (excluding slack):
        i = parent(j)
        V_j = V_i - z_ij * I_branch[i -> j]


    converged = max(|V_new - V_old|) < tol
```

Why this works

Radial structure guarantees $I_{\text{branch}}[i \rightarrow j]$ is unique: only one path connects each bus to the slack.

4-bus radial feeder: setup

slack, $V_1 = 1.00 \angle 0^\circ$

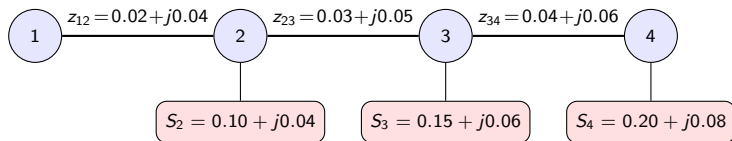

All values are in per-unit on a common base

Total load: $P = 0.45$ pu, $Q = 0.18$ pu. Lines are short and resistive (typical LV feeder). Flat start: $V_2 = V_3 = V_4 = 1.0$.

Iteration 1 – Backward sweep

With $V_i = 1.0$ everywhere, the load currents are $I_i^{\text{load}} = (S_i/V_i)^*$:

Bus	S_i (pu)	I_i^{load} (pu)
2	$0.10 + j0.04$	$0.10 - j0.04$
3	$0.15 + j0.06$	$0.15 - j0.06$
4	$0.20 + j0.08$	$0.20 - j0.08$

Branch currents accumulate from the leaf back to the slack:

$$I_{3 \rightarrow 4} = I_4^{\text{load}} = 0.20 - j0.08$$

$$I_{2 \rightarrow 3} = I_3^{\text{load}} + I_{3 \rightarrow 4} = 0.35 - j0.14$$

$$I_{1 \rightarrow 2} = I_2^{\text{load}} + I_{2 \rightarrow 3} = 0.45 - j0.18$$

Sanity check

$I_{1 \rightarrow 2}$ matches total downstream load $0.45 - j0.18$. At flat start, branch currents are just summed load currents.

Iteration 1 – Forward sweep

Walk from the slack outward, dropping voltage by $z_{ij} \cdot I_{i \rightarrow j}$:


$$\begin{aligned} V_2 &= V_1 - z_{12} \cdot I_{1 \rightarrow 2} = 1.000 - (0.02 + j0.04)(0.45 - j0.18) \\ &= 1.000 - (0.0162 + j0.0144) = 0.984 - j0.014 \end{aligned}$$

$$\begin{aligned} V_3 &= V_2 - z_{23} \cdot I_{2 \rightarrow 3} = 0.984 - j0.014 - (0.03 + j0.05)(0.35 - j0.14) \\ &= 0.984 - j0.014 - (0.0175 + j0.0133) = 0.966 - j0.028 \end{aligned}$$

$$\begin{aligned} V_4 &= V_3 - z_{34} \cdot I_{3 \rightarrow 4} = 0.966 - j0.028 - (0.04 + j0.06)(0.20 - j0.08) \\ &= 0.966 - j0.028 - (0.0128 + j0.0088) = 0.954 - j0.037 \end{aligned}$$

Bus	V_i (complex pu)	$ V_i $ (pu)
2	$0.984 - j0.014$	0.984
3	$0.966 - j0.028$	0.967
4	$0.954 - j0.037$	0.954

Convergence in a few sweeps

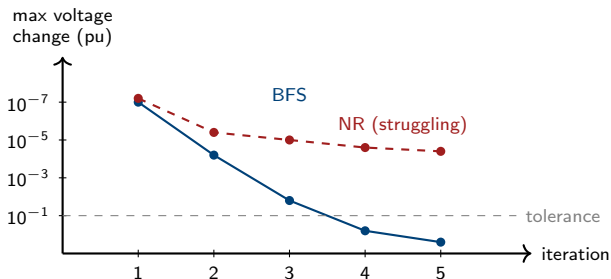

BFS typically

- 3–6 iterations to 10^{-8}
- Cheap per iteration (no Jacobian)
- Reliable on long radial feeders

NR on the same problem

- May not converge from flat start
- Each iteration more expensive
- Better on meshed transmission

Illustrative; exact convergence rate depends on R/X , loading, and topology.

When BFS beats NR (and when it does not)

Scenario	BFS	NR
Long radial LV feeder, heavy load	✓	△
High R/X (e.g. 1–3)	✓	△
Lightly-meshed distribution	✓ *	✓
Heavily-meshed transmission	△	✓
PV-rich feeder with reverse flow	✓ *	✓
Need exact derivatives (sensitivity studies)	△	✓

✓ * requires BFSW (Backward/Forward Sweep with

Walks) or other generalizations.

In pandapower

```
pp.runpp(net, algorithm="bfs") # backward/forward sweep with walks  
pp.runpp(net, algorithm="nr") # default Newton-Raphson
```

Try both on the same network. On a long LV feeder you will often see one converge while the other does not.

The exact branch equation

For a radial branch from bus i to bus j carrying complex power $P_{ij} + jQ_{ij}$ at the sending end:

$$|V_i|^2 - |V_j|^2 = 2(R_{ij} P_{ij} + X_{ij} Q_{ij}) - |Z_{ij}|^2 \cdot |I_{ij}|^2$$

Two terms:

- $2(RP + XQ)$ – the dominant “voltage drop” term, linear in P, Q .
- $|Z|^2 \cdot |I|^2$ – the “loss” term, quadratic in current. Small when V is near 1 and losses are a few percent.

LinDistFlow (Baran & Wu, 1989)

Drop the loss term. Then linearize $|V_i|^2 - |V_j|^2 \approx 2(|V_i| - |V_j|)$ around $|V| \approx 1$:

$$|V_i| - |V_j| \approx R_{ij} P_{ij} + X_{ij} Q_{ij}$$

A clean linear formula. Used everywhere in distribution planning and optimization.

LinDistFlow on the worked example

Apply LinDistFlow to the same 4-bus feeder, using P_{ij}, Q_{ij} = total downstream load on each branch:

Branch	P_{ij} (pu)	Q_{ij} (pu)	$\Delta V = RP + XQ$	$ V_j ^{\text{LinDist}}$
1 $\rightarrow$ 2	0.45	0.18	$0.02(0.45) + 0.04(0.18) = 0.016$	0.984
2 $\rightarrow$ 3	0.35	0.14	$0.03(0.35) + 0.05(0.14) = 0.017$	0.967
3 $\rightarrow$ 4	0.20	0.08	$0.04(0.20) + 0.06(0.08) = 0.013$	0.954

Bus	$ V $ from BFS	$ V $ from LinDistFlow
2	0.984	0.984
3	0.967	0.967
4	0.954	0.954

Why they agree so well

On this feeder, voltages are close to 1.0 pu and losses are a fraction of a percent. The neglected $|Z|^2|I|^2$ term is in the 4th decimal place.

When LinDistFlow is accurate, and when it lies

Accurate within $\sim 0.5\%$ when:

- All $|V_i| \in [0.95, 1.05]$
- Losses $< 2\text{--}3\%$ of total flow
- No large reverse flow
- No dominant $|I|^2$ heating

Becomes optimistic when:


- Heavy PV generation pushing voltages above 1.05
- Long feeder with $|V|$ near 0.92–0.93
- High line current $\rightarrow |I|^2 R$ losses matter
- Capacitor banks switching $\rightarrow Q$ changes abruptly

Where you will see it


LinDistFlow underlies many distribution OPF formulations, DER siting/sizing problems, and Volt/VAR optimization. We will use BFS in this course because we want absolute voltage values, but the linear form is what makes large planning problems tractable.

What DER changes

Without DER

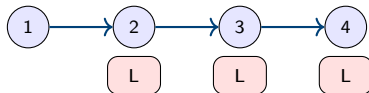

With end-of-feeder PV

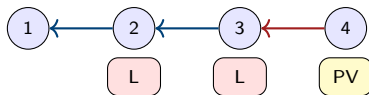

- Without DER: power flows substation $\rightarrow$ loads. Voltage decreases away from substation.
- With heavy DER at the end of the feeder: power can flow *toward* the substation. Voltage *rises* near the DER.

Voltage rise – a numerical example

A 2-bus toy feeder, LV characteristics: $z = 0.05 + j0.05$ pu, $V_1 = 1.00$.

Case	Net injection at bus 2	$\Delta V = (RP + XQ)/V$	$ V_2 $
(a) 0.5 pu load only	-0.50 pu	+0.025	0.975 pu
(b) 0.5 pu PV, 0.5 pu load (offset)	0.00 pu	0.000	1.000 pu
(c) 1.5 pu PV, 0.5 pu load (export 1.0)	+1.00 pu	-0.050	1.050 pu
(d) 2.0 pu PV, 0.5 pu load (export 1.5)	+1.50 pu	-0.075	1.075 pu

The pattern

Case (a) is the classical low-voltage problem: load $\rightarrow$ voltage drops.

Case (d) is the modern high-voltage problem: PV $\rightarrow$ voltage rises past 1.05 pu.

Same feeder, opposite violations. A simple “low-voltage check” is no longer enough.

Reverse power flow and what it breaks

When DER injection at a bus exceeds local load, net power flows *toward* the substation. Several consequences:

- Voltage rises along the upstream path.
- Some protection relays assume one-directional flow.
- Transformer tap controllers may move the wrong way.
- Loss calculations need to be reconsidered.

Magnitude in practice

At 30–50% PV penetration on a typical LV feeder, the substation can already see negative net flow at midday on clear weekends.


Connection to this course

Reverse flow + voltage rise = a violation mode the N-1 screening model must learn. Week 4 of the project labels both kinds.

Hosting capacity in one slide

Question: how much DER can be added to a feeder before *any* voltage or thermal limit is violated?


$\max_i |V_i|$ at minimum load

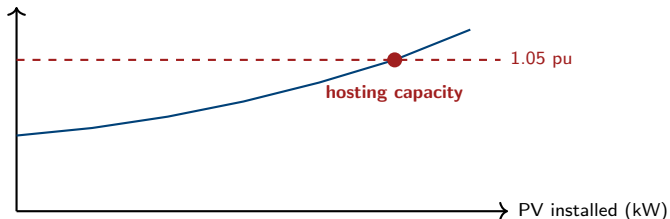

Definitions

- **Hosting capacity** = the PV size at which the first constraint becomes binding under the worst-case operating condition (typically: maximum PV, minimum load).
- It is determined by either voltage rise or thermal overload, whichever comes first.
- Computing it requires the same N-1-style PF scans we will use in Weeks 3–4 of the project.

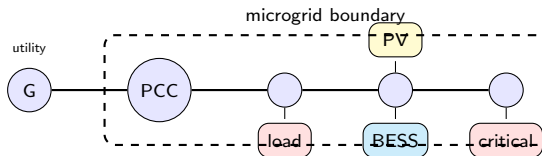
Microgrid = distribution + control boundary



What “microgrid” adds on top of a distribution feeder

- Defined electrical boundary at the Point of Common Coupling (PCC).
- Internal generation that can support load when the utility is disconnected.
- Supervisory control (energy management system).
- Often: critical loads with higher reliability requirements.

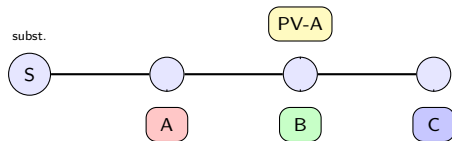Why distribution is rarely truly balanced



Sources of phase asymmetry on LV / microgrid feeders:

- Single-phase loads (most residential consumers connect to one phase only).
- Single-phase rooftop PV (the inverter is connected to the homeowner's phase).
- Single-phase EV chargers, water heaters, ovens.
- Untransposed lines – transposition is rarely worth the cost at LV.
- Asymmetric three-phase loads (one phase under heavy use, others idle).

Implication

Phase A could drop to 0.92 pu while phase B sits at 1.01 pu and phase C at 1.03 pu. *Average* voltage looks fine. Balanced power flow happily reports “no violation”. Phase A is in violation.

Teaser of L04

What L04 will add to today's machinery:

- Symmetrical components: positive, negative, zero.
- Sequence-domain formulation of the PF.
- Voltage Unbalance Factor (VUF).
- `pandapower.runpp_3ph` as the practical solver.
- Five violation types (incl. VUF).

What stays from L02

- Radial topology still simplifies things.
- BFS generalizes to three-phase.
- Voltage rise behavior still applies per-phase.
- Hosting capacity becomes per-phase.

Bridge

L02 said: “transmission tools do not transfer to distribution.” L04 will say: “single-phase distribution tools do not transfer to phase-aware distribution.” Same kind of failure of an unstated assumption.

Homework

Required

- 1 Reproduce the 4-bus radial example in pandapower. Use `pp.create_line_from_parameters` with R, X consistent with the per-unit values in the slides.
- 2 Run both `pp.runpp(net, algorithm="bfs")` and `pp.runpp(net, algorithm="nr")`. Confirm `net.converged` for both and verify $|V_i|$ matches the worked example to 3 decimal places.
- 3 Multiply all line impedances by 5. Re-run. Which bus moves the most? Why?
- 4 Replace the load at bus 4 with a 1.0 pu PV sgen. Find the smallest PV injection that pushes $|V_4|$ above 1.05.

Optional

- 1 Implement BFS yourself in ~ 30 lines of `numpy` and compare to pandapower's `bfs`.
- 2 Plot the voltage profile $|V_i|$ vs bus index for load levels 0%, 50%, 100%, 150% of the slide values.
- 3 Find the hosting capacity (max PV at bus 4 before any violation) under the worst-case minimum load.

Exit checklist

- 1 ✓ I can explain in one sentence why transmission solvers struggle on distribution feeders.
- 2 ✓ I can sketch the side-by-side topology of a transmission vs distribution network.
- 3 ✓ I can write the simplified voltage drop $\Delta V = (RP + XQ)/V$ and explain when it lies.
- 4 ✓ I can describe one backward sweep and one forward sweep in BFS on a small radial feeder.
- 5 ✓ I can choose between `algorithm="nr"` and `algorithm="bfsw"` for a given network.
- 6 ✓ I can describe how end-of-feeder PV causes voltage rise.
- 7 ✓ I can define hosting capacity in two sentences.
- 8 ✓ I know exactly which assumption from L02 will break in L04 (single-phase equivalent).

References

- **Kersting**, *Distribution System Modeling and Analysis* (4th ed., 2017). The canonical distribution PF textbook.
- **Baran & Wu, 1989**. *Optimal Capacitor Placement on Radial Distribution Systems*, IEEE TPD. The DistFlow / LinDistFlow paper.
- **Cespedes, 1990**. *New Method for the Analysis of Distribution Networks*, IEEE TPD. Classical BFS reference.
- **Shirmohammadi et al., 1988**. *A Compensation-Based Power Flow Method for Weakly Meshed Distribution Networks*, IEEE TPS.
- **Bollen & Hassan, Integration of Distributed Generation in the Power System** (Wiley, 2011). Voltage rise, hosting capacity.
- **IEEE Std 1547-2018**, *Standard for Interconnection of DER*. Voltage and frequency ride-through requirements.
- **pandapower docs**: <https://pandapower.readthedocs.io> – look for “BFSW” under power-flow algorithms.